

# **Module 4: Choosing Between Verilog Data Types**




## Lab 4-1 Modeling a Data Driver

**Objective:** To use a Verilog literal value to describe a parameterized-width bus driver.

---

The driver output is equal to the input value when enabled (*data\_en* is true) and is high-impedance when not enabled (*data\_en* is false).

 In this lab, you create a data driver as per the specification and verify it using the provided testbench. Please make sure to use the same variable name as the ones shown in block diagrams.



### Specifications

- ◆ *data\_in* and *data\_out* are both parameterized widths of 8-bit.
- ◆ If *data\_en* is high, the input *data\_in* is passed to the output *data\_out*.
- ◆ Otherwise, *data\_out* is high impedance.

### Designing a Data Driver

1. Change to the *lab5-drvr* directory and examine the following files.

driver_test.v	Driver test
---------------	-------------

2. Create the *driver.v* file, and using your favorite editor, describe the driver module named “*driver*”.
3. Parameterize the driver input and output width and assign a default value of 8.

## Verifying the Driver Design

1. Using the provided testbench module, check your driver design using the following command with VCS.

```
vcs driver.v driver_test.v (Batch Mode)
```

or

```
vcs driver.v driver_test.v -gui -access +rwc ( GUI Mode)
```

2. You might find it easier to list all the files and simulation options in a text file and pass the file into the simulator using the `-f vcs` option.

```
vcs-f filelist.txt -access rwc
```

You should see the following results.

```
At time 1 data_en=0 data_in=xxxxxxx data_out=zzzzzzzz
At time 2 data_en=1 data_in=01010101 data_out=01010101
At time 3 data_en=1 data_in=10101010 data_out=10101010
TEST PASSED
```

3. Correct your driver design as needed.