


# **Module 6: Making Procedural Statements**


 
## Lab 6-1 Modeling a Controller

**Objective:** To use the Verilog case statement to describe a controller.

The controller generates all control signals for the VeriRISC CPU. The operation code, fetch-and-execute phase, and whether the accumulator is zero determine the control signal levels.



### Specifications


- ♦ The controller is clocked on the rising edge of `clk`.
- ♦ `rst` is synchronous and active high.
- ♦ `zero` is an **input** which is 1 when the CPU accumulator is zero and 0 otherwise.
- ♦ `opcode` is a 3-bit **input** for CPU operation, as shown in the following table.

Opcode/ Instruction	Opcode Encoding	Operation	Output
HLT	000	PASS A	$\text{in\_a} \Rightarrow \text{alu\_out}$
SKZ	001	PASS A	$\text{in\_a} \Rightarrow \text{alu\_out}$
ADD	010	ADD	$\text{in\_a} + \text{in\_b} \Rightarrow \text{alu\_out}$
AND	011	AND	$\text{in\_a} \& \text{in\_b} \Rightarrow \text{alu\_out}$
XOR	100	XOR	$\text{in\_a} \wedge \text{in\_b} \Rightarrow \text{alu\_out}$
LDA	101	PASS B	$\text{in\_b} \Rightarrow \text{alu\_out}$
STO	110	PASS A	$\text{in\_a} \Rightarrow \text{alu\_out}$
JMP	111	PASS A	$\text{in\_a} \Rightarrow \text{alu\_out}$

- ♦ There are 7 single-bit **outputs**, as shown in this table.

Output	Function
sel	select
rd	memory read
ld_ir	load instruction register
halt	halt
inc_pc	increment program counter
ld_ac	load accumulator
ld_pc	load program counter
wr	memory write
data_e	data enable

 - ♦ The controller has a single-bit phase input with a total of 8 phases processed. Phase transitions are unconditional, i.e., the controller passes through the same 8-phase sequence, from INST\_ADDR to STORE, every 8 clk cycles. The reset state is INST\_ADDR.



- ♦ The controller outputs will be decoded w.r.t phase and opcode, as shown in this table.

Outputs	Phase							Notes	
	INST_ADDR	INST_FETCH	INST_LOAD	IDLE	OP_ADDR	OP_FETCH	ALU_OP	STORE	
sel	1	1	1	1	0	0	0	0	ALU_OP = 1 if opcode is ADD, AND, XOR or LDA
rd	0	1	1	1	0	ALUOP	ALUOP	ALUOP	
ld_ir	0	0	1	1	0	0	0	0	
halt	0	0	0	0	HALT	0	0	0	
inc_pc	0	0	0	0	1	0	SKZ && zero	0	
ld_ac	0	0	0	0	0	0	0	ALUOP	
ld_pc	0	0	0	0	0	0	JMP	JMP	
wr	0	0	0	0	0	0	0	STO	
data_e	0	0	0	0	0	0	STO	STO	

## Designing a Controller

1. Change to the *lab7-ctrl* directory and examine the following files.

controller_test.v	Controller test
filelist.txt	File listing all modules to simulate

2. Use your favorite editor to create the *controller.v* file and describe the controller module named “*control*”.
3. Declare a reg for each of these intermediate terms and establish their value immediately before entering the case statement.

## Verifying the Controller Design

1. Using the provided test module, check your controller design using the following command with Xcelium™.

```
xrun controller.v controller_test.v (Batch Mode)
```

or

```
xrun controller.v controller_test.v -gui -access +rwc ( GUI Mode)
```

2. You might find it easier to list all the files and simulation options in a text file and pass the file into the simulator using the `-f xrun` option.

```
xrun -f filelist.txt -access rwc
```

You should see the following results.

```
Testing opcode HLT phase 0 1 2 3 4 5 6 7
Testing opcode SKZ phase 0 1 2 3 4 5 6 7
Testing opcode ADD phase 0 1 2 3 4 5 6 7
Testing opcode AND phase 0 1 2 3 4 5 6 7
Testing opcode XOR phase 0 1 2 3 4 5 6 7
Testing opcode LDA phase 0 1 2 3 4 5 6 7
Testing opcode STO phase 0 1 2 3 4 5 6 7
Testing opcode JMP phase 0 1 2 3 4 5 6 7
TEST PASSED
```

3. Correct your controller design as needed.

